

AC/DC Converter: Stereo Speaker

Raktim Gautam Goswami and Abhishek Bairagi

CONTENTS

| | | |
|-----|-----------------------------|---|
| 1 | Components | 1 |
| 2 | Connections | 1 |
| 3 | Regulator | 1 |
| 3.1 | Ripple Filter | 1 |
| 3.2 | Voltage Regulator | 1 |
| 4 | Audio amplification | 2 |

Abstract—In this manual we will be making a stereo speaker which will take audio input, amplify it and give output through speaker.

1 COMPONENTS

| Component | Value | Quantity |
|-----------------------|------------------------------|----------|
| Step Down Transformer | 230V AC - 12V AC - 750 mA | 1 |
| Diode | | 4 |
| Capacitor | 1000 μ F | 1 |
| Capacitor | 220 μ F | 4 |
| Voltage Regulator | LM7809 | 1 |
| Jumper Wires | M-M | 20 |
| Audio Amplifier ICs | LM386 | 2 |
| Speakers | | 2 |
| Audio Jack | | 1 |
| Potentiometer | 10k OHM | 2 |
| PCB | | 1 |

TABLE I

2 CONNECTIONS

Problem 2.1. Connect the 230V AC supply to the input of the step-down transformer as shown in Fig 2.1.

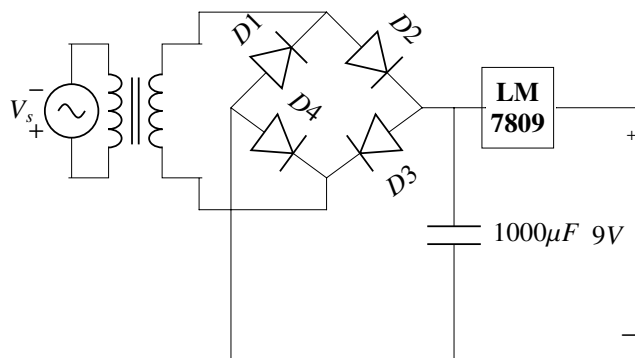


Fig. 2.1: AC-DC circuit diagram

Problem 2.2. Verify that the output of the transformer is 12 V AC. What is the frequency?

Problem 2.3. Connect the 4 diodes in bridge.

Problem 2.4. Connect the output of the transformer to the to the junction of diodes D1, D2 and D3 , D4 .

Problem 2.5. Measure the voltage and frequency at the input and output of transformer.

Solution: The input voltage is 230V @ 50 Hz and output of transformer is approximately 20V @ 50 Hz.

Problem 2.6. The observed output of the Bridge Rectifier between junctions of D1,D4 and D2,D3 on oscilloscope is as shown in Fig. 2.6.

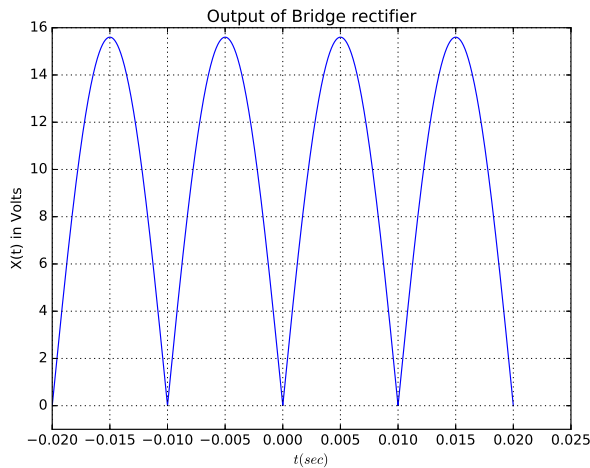


Fig. 2.6: Rectified Wave

3 REGULATOR

3.1 Ripple Filter

Problem 3.1. The capacitor in Fig. 2.1 acts as a ripple filter. Sketch its output.

Solution: See Fig. 3.1.

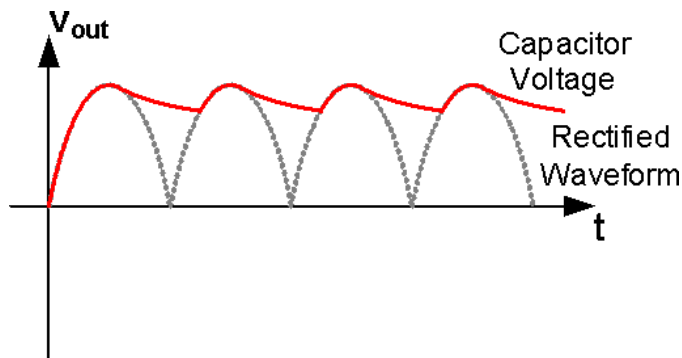


Fig. 3.1: Rectified Wave with Capacitive filter

3.2 Voltage Regulator

Problem 3.2. Connect pin 1 and pin 2 of LM7809 to positive and Ground terminals of 220 μ F capacitor and pin 3 to the positive of another 220 μ F capacitor. Connect other end of capacitor to ground. See Figs. 3.2 and 3.3

Problem 3.3. Measure the Voltage across pin 3 and Ground of LM7809. What do you observe?

Solution: The output voltage is observed to be 9V.

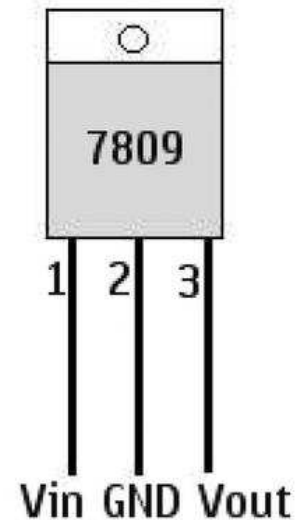


Fig. 3.2: LM7809

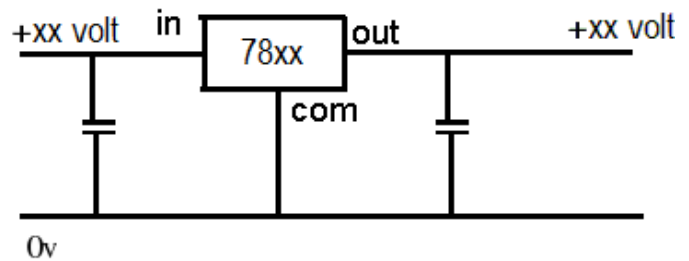


Fig. 3.3: LM 7809 connections

4 AUDIO AMPLIFICATION

Problem 4.1. Connect the 9V obtained from the previous circuit to pin 6 and ground to pin 2 and 4 of LM386 IC.

Problem 4.2. Connection points for the audio jack are as shown in Fig. 4.2

Problem 4.3. Connect one input from audio jack to pin 3 of LM386 IC with a variable resistor in series (you can use potentiometer instead of variable resistor). See Fig. 4.3.

Problem 4.4. Connect one wire of speaker to pin 5 of LM386 through a 220 μ F (C1) capacitor and other to ground.

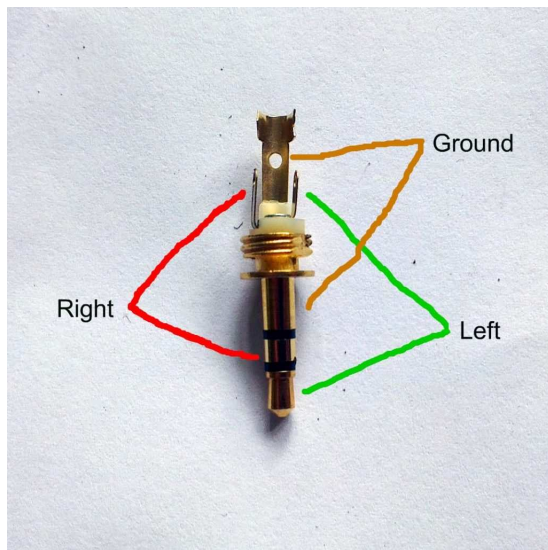


Fig. 4.2: Audio Jack connection points

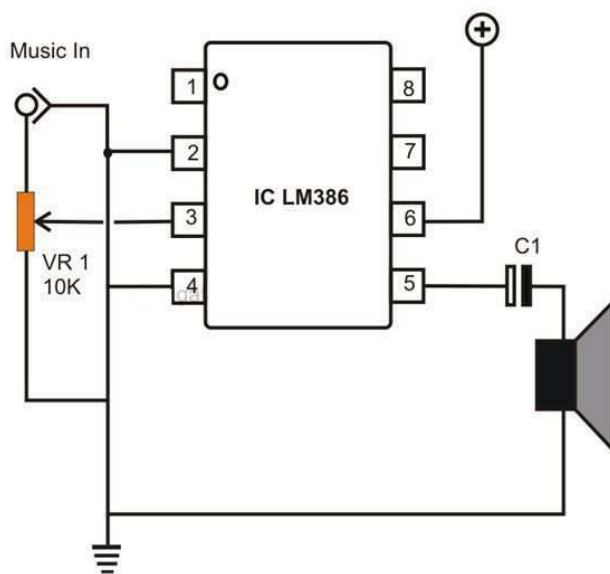


Fig. 4.3: LM386

Problem 4.5. Make the same circuit with another LM386 IC (This time use the other input of audio jack and connect remaining wire of audio jack to ground).

Problem 4.6. Now connect audio jack to an input device and turn on power supply. Try changing volume by potentiometer.